

[illegible]

TITLE: common-collector-1	Project
Description:	
Simple amplifier operation. As R1 is adjusted test point voltage is increased until the LED lights. This is a "non-inverting" amplifier. The output voltage is "one diode drop less" than the input voltage.	
Author, license: Pete Soper - Durham Makerspace https://creativecommons.org/publicdomain/zero/1.0/	
Repo: https://github.com/splatspace/currentevent	
Date: 4/8/17 11:31 AM	



at: Current Event Workshops

oint two voltage rises to the LED
nverting" amplifier. When turned on the
than the base voltage at test point one

