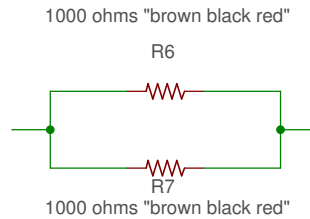



How many ohms of resistance from top to bottom?

QUESTION 1




How many ohms of resistance from left to right?

QUESTION 2

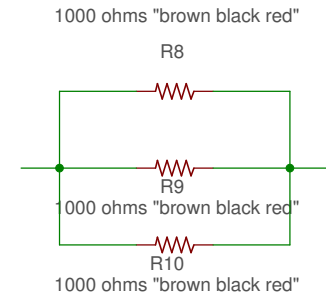


How many ohms of resistance from left to right?


QUESTION 3

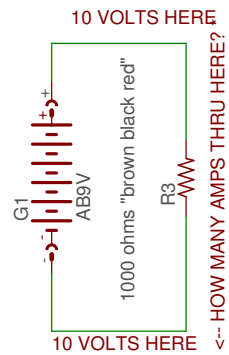

QUESTION 4

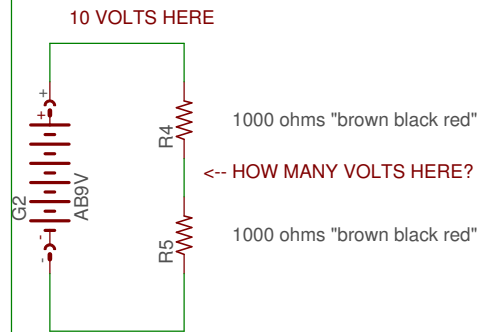

QUESTION 5

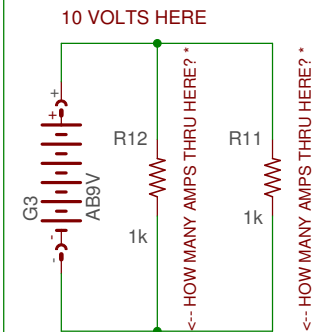

QUESTION 6

\* CONVENTIONAL CURRENT FLOW USED THROUGHOUT